

PHYS 122L Experiment 8


Circuits

Brandon Tsang

February 12, 2020

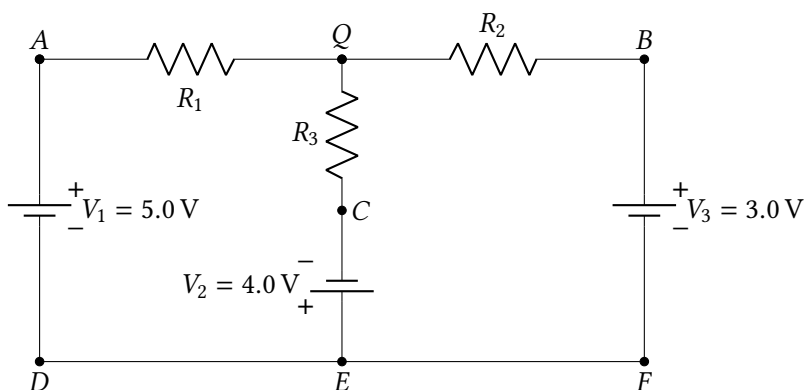Part A: Investigation of a multiloop DC circuit

The following measurements will be made on this circuit:



Resistances	Voltage drops	Current
$R_1 = 991(0) \, \Omega$	$V_{R_1} = 5.57(2) \, \text{V}$	$I_{R_1} = 0.5623 \, \text{mA}$
$R_2 = 2162(5) \, \Omega$	$V_{R_2} = 3.55(8) \, \text{V}$	$I_{R_2} = 0.1645 \, \text{mA}$
$R_3 = 482(2) \, \Omega$	$V_{R_3} = -3.50(4) \, \text{V}$	$I_{R_3} = -0.7267 \, \text{mA}$

Summing the currents calculated above, we get that $\sum I = 0.0001 \, \text{mA}$, which is very close to zero. This confirms Kirchhoff's current law.

For the left loop:

$$V_{AQ} = 5.57(3) \, \text{V}$$

$$V_{QC} = 3.50(4) \, \text{V}$$

$$V_{CE} = -3.99(8) \, \text{V}$$

$$V_{DA} = -5.08(2) \, \text{V}$$

$$\sum V = -0.003 \, \text{V}$$

For the right loop:

$$V_{QB} = -3.55(8) \, \text{V}$$

$$V_{BF} = 3.06(7) \, \text{V}$$

$$V_{EC} = 3.99(8) \, \text{V}$$

$$V_{CQ} = -3.50(4) \, \text{V}$$

$$\sum V = 0.003 \, \text{V}$$

For the outer loop:

$$V_{AQ} = 5.57(3) \, \text{V}$$

$$V_{QB} = -3.55(8) \, \text{V}$$

$$V_{BF} = 3.06(7) \, \text{V}$$

$$V_{DA} = -5.08(3) \, \text{V}$$


$$\sum V = -0.001 \, \text{V}$$

For all three loops, $\sum V \approx 0$. This confirms Kirchhoff's voltage law.

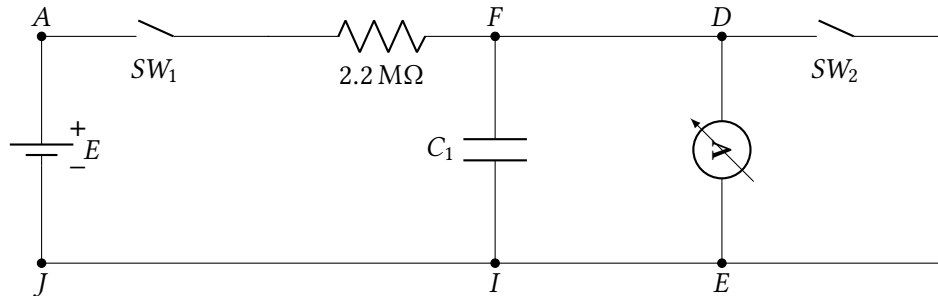Part B: Charge and discharge of a capacitor

Charge of a capacitor


The following measurements will be made on this circuit:



All time values have an uncertainty of $\pm 0.01\text{ s}$.

Voltage (V)	Time (s)			Average time (s)	$\frac{E'}{E'-V}$
	1	2	3		
0.5	2.85	2.82	2.61	2.76	1.14
1.0	5.59	5.92	5.79	5.77	1.33
1.5	9.09	8.97	9.21	9.09	1.60
2.0	13.06	12.95	12.68	12.90	2.00
2.5	18.14	18.15	18.09	18.12	2.67
3.0	25.10	25.36	25.33	25.26	4.00
3.5	37.98	37.49	37.70	37.72	8.00

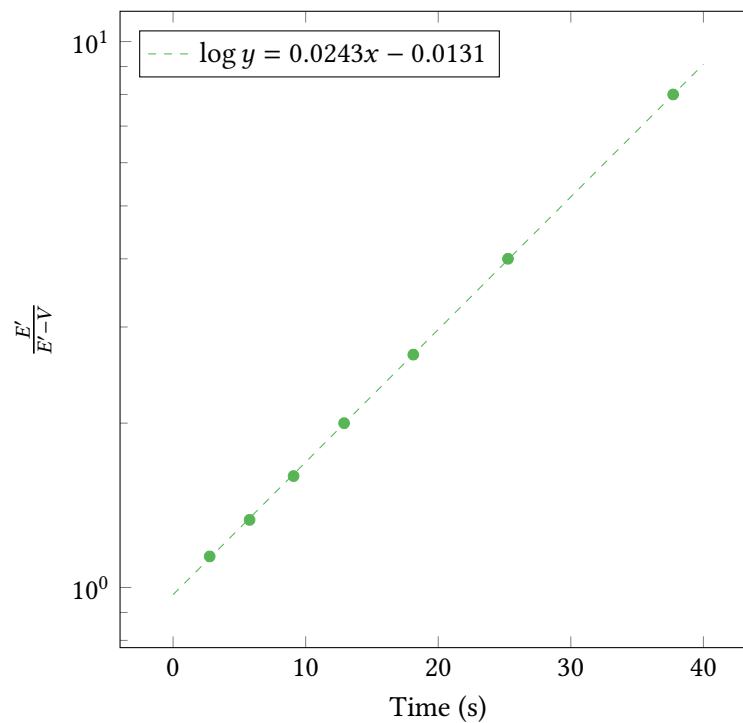Plotting $\frac{E'}{E'-V}$ vs. t on a semi-log graph, we get:



Notes about the above graph:

- The error bars are too small to be shown.
- The dashed line is a regression of the data.

The slope of the line is $m = 0.0243$. Using this, we can calculate C_1 :

$$m = \frac{\log e}{R'C_1} \quad (1)$$

$$\frac{1}{C_1} = \frac{mR'}{\log e} \quad (2)$$

$$C_1 = \frac{\log e}{mR'} \quad (3)$$

To calculate R' :

$$R' \equiv \frac{R_M}{R_M + R} \cdot R \quad (4)$$

$$= \frac{10.5 \text{ M}\Omega}{10.5 \text{ M}\Omega + 2.2 \text{ M}\Omega} \cdot 2.2 \text{ M}\Omega \quad (5)$$

$$= 1.82 \text{ M}\Omega \quad (6)$$

$$= 1.82 \times 10^6 \Omega \quad (7)$$

Plugging this back into Equation 3:


$$C_1 = \frac{\log e}{(0.0243 \text{ s}^{-1})(1.82 \times 10^6 \Omega)} \quad (8)$$

$$= 9.82 \text{ s } \Omega^{-1} \quad (9)$$

$$= 9.82 \text{ F} \quad (10)$$


Discharge of a capacitor

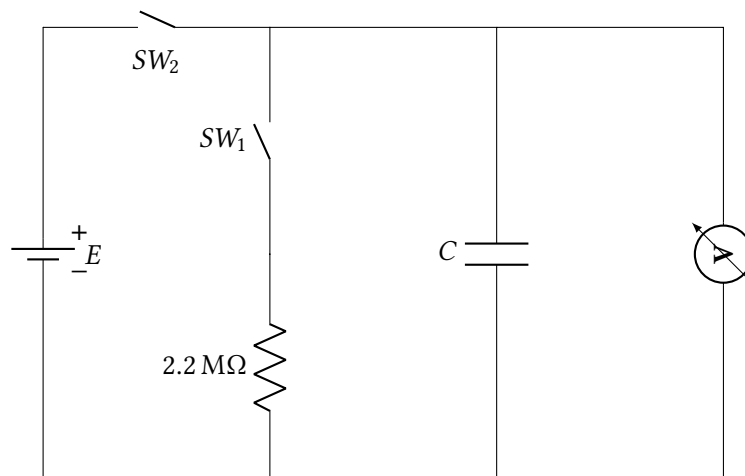The following measurements will be made on this circuit:



Voltage (V)	$\frac{V}{V_0}$	Time (s)
4.00	0.89	1.56
3.50	0.78	2.52
3.00	0.67	3.65
2.50	0.56	5.10
2.00	0.44	6.32
1.50	0.33	8.56
1.00	0.22	12.31

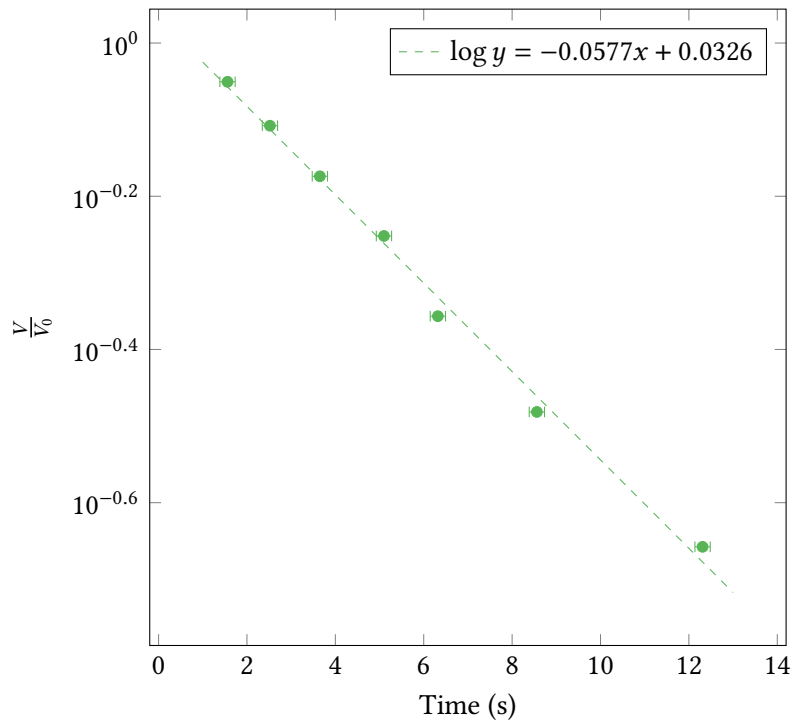Plotting $\frac{V}{V_0}$ vs. time on a semi-log graph:



The slope of the dashed regression line is $m = -0.0577$. Using this, we can calculate C_2 :

$$m = \frac{\log e}{R'C_2} \quad (11)$$

$$\frac{1}{C_2} = \frac{mR'}{\log e} \quad (12)$$

$$C_2 = \frac{\log e}{mR'} \quad (13)$$

$$= \frac{\log e}{(-0.0577 \text{ s}^{-1})(1.82 \times 10^6 \Omega)} \quad (14)$$

$$= -4.14 \Omega \text{ s}^{-1} \quad (15)$$

$$= -4.14 \text{ F} \quad (16)$$

Part C: Capacitors in series and parallel

[incomplete]